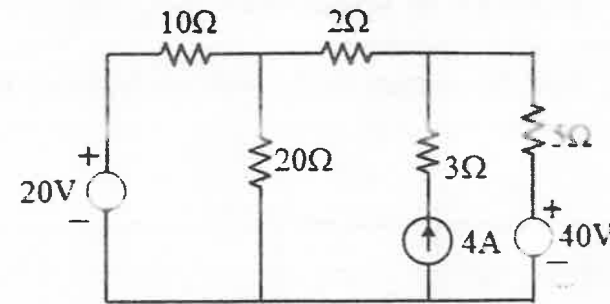


**PART - C (1 × 15 = 15 Marks)**  
Answer ANY ONE Question

Marks BL CO PO

26. Applying superposition theorem for the circuit shown below, determine the voltage drop across the  $2\Omega$  resistor.



27. Simplify the following Boolean expressions using k-map and implement the simplified expressions using logic gates.

$$Y(A, B, C, D) = \sum_m(0, 1, 2, 4, 5, 7, 8, 9, 10, 12, 13)$$

$$Y(A, B, C, D) = \pi_M(3, 6, 11, 14, 15)$$

\*\*\*\*\*

Reg. No.

**B.Tech. / M.Tech (Integrated) DEGREE EXAMINATION, MAY 2023**  
First and Second Semester

**21EES101T – ELECTRICAL AND ELECTRONICS ENGINEERING**  
(For the candidates admitted from the academic year 2021 - 2022 & 2022 - 2023)

Note:

- (i) **Part - A** should be answered in OMR sheet within first 40 minutes and OMR sheet should be handed over to hall invigilator at the end of 40<sup>th</sup> minute.  
(ii) **Part - B and Part - C** should be answered in answer booklet.


Time: 3 Hours

Max. Marks: 75

**PART - A (20 × 1 = 20 Marks)**

Answer ALL Questions

- |                                                                                                                                                                                                             | Marks | BL | CO | PO |
|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------|----|----|----|
| 1. A 100 W lamp is connected across 220 V DC supply. Determine the value of current drawn by the lamp?<br>(A) 2.5A (B) 10A<br>(C) 0.45A (D) 5A                                                              | 1     | 2  | 1  | 1  |
| 2. To neglect the voltage source in Thevenin's theorem, the terminal across the sources are _____.<br>(A) Replaced by load resistance (B) Replaced by capacitance<br>(C) Short circuited (D) Open circuited | 1     | 1  | 1  | 1  |
| 3. In a circuit with pure inductance, the current _____ the voltage by 90°.<br>(A) Leads (B) Lags<br>(C) In phase (D) Greater than and equal                                                                | 1     | 1  | 1  | 1  |
| 4. The nodal method of circuit analysis is based on _____.<br>(A) Thevenin's theorem (B) Norton's theorem<br>(C) Kirchoff voltage law (D) Kirchoff current law                                              | 1     | 1  | 1  | 1  |
| 5. The knee voltage of silicon diode is _____.<br>(A) 0.2 V (B) 0.7 V<br>(C) 0.8 V (D) 1.0 V                                                                                                                | 1     | 1  | 2  | 1  |
| 6. Which among the following is a current controlled device?<br>(A) BJT (B) MOSFET<br>(C) JFET (D) Diode                                                                                                    | 1     | 1  | 2  | 1  |
| 7. The algebraic function of XOR gate is _____.<br>(A) $xy' + x'y$ (B) $xy + x'y'$<br>(C) $xy + x'y$ (D) $xy + xy'$                                                                                         | 1     | 1  | 2  | 1  |
| 8. FPGA stands for _____.<br>(A) Flexible Programmable Gate Array (B) Flexible Programmable Gate Acceleration<br>(C) Field Programmable Gate Accelerator (D) Field Programmable Gate Array                  | 1     | 1  | 2  | 1  |

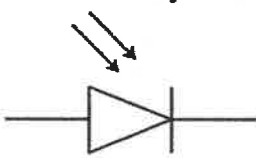
9. The transformer core is made up of laminations to reduce  
(A) Eddy current losses (B) Iron losses  
(C) Stray losses (D) Hysteresis loss
10. The function of a commutator in DC generator is to \_\_\_\_\_  
(A) Convert DC to DC (B) Convert AC to DC  
(C) Convert AC to AC (D) Convert DC to AC
11. In a three phase induction motor, the three phase winding R, Y, B are connected in \_\_\_\_\_.  
(A) Series (B) Parallel  
(C) Series and parallel (D) Star
12. Stepper motor is a \_\_\_\_\_ device.  
(A) Mechanical (B) Analog  
(C) Incremental (D) Storage
13. Moving coil instruments are used to measure  
(A) DC quantity only (B) AC quantity only  
(C) Both AC and DC quantity (D) Either AC or DC
14. The below symbol represents \_\_\_\_\_ device.  
  
(A) LED (B) LCD  
(C) Photodiode (D) Laser diode
15. Which of the following represents active transducer?  
(A) Strain gauge (B) LVDT  
(C) Thermistor (D) Thermocouple
16. What is the principle employed in operation of LVDT?  
(A) Mutual inductance (B) Self inductance  
(C) Permeance (D) Reluctance
17. What is the frequency of AC supply followed in India?  
(A) 50 Hz (B) 60 Hz  
(C) 40 Hz (D) 75 Hz
18. Which of the following is a non-renewable energy resource?  
(A) Solar power (B) Wind power  
(C) Thermal power (D) Tidal power
19. Earthing is an essential protection to provide against \_\_\_\_\_.  
(A) Overloading (B) Voltage fluctuation  
(C) Heating issues (D) Danger of electric shock

20. Electric vehicles and hybrid vehicles have the following components common EXCEPT:  
(A) Battery (B) Electronic control unit  
(C) Motor (D) Internal combustion engine

**PART – B (5 × 8 = 40 Marks)**

Answer ALL Questions

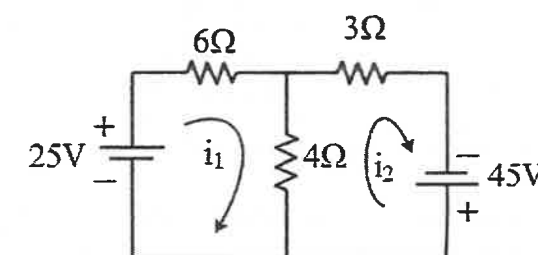21. a. Applying mesh analysis, find the current in the various resistors in the circuit shown below:



(OR)

- b. An inductive coil takes 10A and dissipates 1000W when connected to a supply of 250V, 25Hz. Calculate the impedance, resistance, reactance and the power factor.
22. a. Sketch the circuit diagram and output characteristics of JFET and explain its operation.  
(OR)  
b. With neat circuit diagram, discuss the operation of linear voltage regulator.
23. a. Describe the construction and working principle of BLDC motor with neat diagram.  
(OR)  
b. Briefly explain the factors to be considered for the selection of drives for cranes.
24. a. With neat sketch, comment on the construction and working principle of an instrument which is used to measure only dc quantities.  
(OR)  
b. Write short notes on:  
(1) Thermistor  
(2) Thermocouple
25. a. Describe the simple layout of electrical power system with neat sketch.  
(OR)  
b. With neat diagram, explain the working of a fuel cell.