

B.Tech / M.Tech (Integrated) DEGREE EXAMINATION, JANUARY 2024

First Semester

21EES101T - ELECTRICAL AND ELECTRONICS ENGINEERING

(For the candidates admitted during the academic year 2022-2023 onwards)

Note:

i. **Part - A** should be answered in OMR sheet within first 40 minutes and OMR sheet should be handed over to hall invigilator at the end of 40th minute.

ii. **Part - B** and **Part - C** should be answered in answer booklet.

Time: 3 Hours

Max. Marks: 75

PART - A (20 × 1 = 20 Marks)

Answer all Questions

Marks BL CO

- | | | | | |
|--|---|---|---|---|
| 1. Thevenin's resistance is found by _____
(A) Shorting all voltage sources
(C) Shorting all voltage sources and opening all current sources | (B) Opening all current sources
(D) Opening all voltage sources and shorting all current sources | 1 | 1 | 1 |
| 2. The internal resistance for the maximum transfer of power should be
(A) equal to load resistance
(C) zero | (B) greater than load resistance
(D) lesser than load resistance | 1 | 1 | 1 |
| 3. The 2ohm and 3 ohm resistor are in series the equivalent resistance is
(A) 1.2 ohm
(C) 4.2 ohm | (B) 5 ohm
(D) 9 ohm | 1 | 3 | 1 |
| 4. In a star connected system, the current flowing through the line is
(A) Greater than the phase current
(C) Lesser than the phase current | (B) Equal to the phase current
(D) zero | 1 | 1 | 1 |
| 5. How many AND gates are required to realize A.B+C.D+E
(A) 2
(C) 3 | (B) 4
(D) 1 | 1 | 1 | 1 |
| 6. When both inputs are HIGH, output Y will be ____ (HIGH, LOW) and the LED will ____ (light, not light).
(A) Low, Light
(C) High, Not Light | (B) High, Light
(D) Low, Not Light | 1 | 2 | 2 |
| 7. The structure of the IGBT is a _____
(A) P-N-P structure connected by a MOS gate
(C) P-N-P-N structure connected by a MOS gate | (B) N-N-P-P structure connected by a MOS gate
(D) N-P-N-P structure connected by a MOS gate | 1 | 1 | 2 |
| 8. An SCR is a _____
(A) four layer, four junction device
(C) four layer, two junction device | (B) four layer, three junction device
(D) three layer, single junction device | 1 | 1 | 2 |
| 9. Thin laminations are used in a machine in order to reduce
(A) Eddy current losses
(C) Copper losses | (B) Hysteresis losses
(D) Interference | 1 | 1 | 3 |
| 10. Commutator in DC generator is used for
(A) collecting of current
(C) increase efficiency | (B) reduce losses
(D) convert AC armature current in to DC | 1 | 1 | 3 |


- | | | | |
|--|--|---|---|
| 11. The frame of an induction motor is usually made of | 1 | 1 | 3 |
| (A) Silicon steel | (B) Cast iron | | |
| (C) Aluminum | (D) Bronze | | |
| 12. An elevator drive is required to operate in _____ | 1 | 1 | 3 |
| (A) one quadrant only | (B) two quadrants. | | |
| (C) three quadrants. | (D) four quadrants. | | |
| 13. LEDs fabricated from the gallium arsenide emit radiation in the | 1 | 1 | 4 |
| (A) Visible Range | (B) Infrared Region | | |
| (C) Ultra violet Region | (D) Ultrasonic Region | | |
| 14. A device consists of a photo transistor and a led is _____ | 1 | 1 | 4 |
| (A) Photo diode | (B) Opto coupler | | |
| (C) Opto isolator | (D) Photo multiplier | | |
| 15. In Ultrasonic proximity sensors the distance between the sensor and the target is determined by | 1 | 1 | 4 |
| (A) time taken by reflected light to reach back to sensor. | (B) time taken by the sound to reflect back to the sensor. | | |
| (C) measuring voltage at the output. | (D) measuring changes in output current. | | |
| 16. _____ is the principle of operation of LVDT | 1 | 1 | 4 |
| (A) Mutual inductance | (B) Self-inductance | | |
| (C) Permanence | (D) Reluctance | | |
| 17. For proper earthing, what should be the maximum value of earth resistance while carrying out the testing of the earth's continuity path? | 1 | 1 | 5 |
| (A) 1 ohm | (B) 2 ohm | | |
| (C) 5 ohm | (D) 10 ohm | | |
| 18. Identify the device which is used to give the signal to the circuit breaker at the time of fault | 1 | 1 | 5 |
| (A) Fuse | (B) Isolator | | |
| (C) Relay | (D) CT | | |
| 19. Electric vehicles and inductionhybrid vehicles have the following components in common except _____ | 1 | 1 | 5 |
| (A) Battery | (B) ECU | | |
| (C) Generator | (D) internal combustion engine | | |
| 20. The highest transmission voltage used in India is | 1 | 1 | 5 |
| (A) 230 kV | (B) 1100 kV | | |
| (C) 765 kV | (D) 400 kV | | |

PART - B (5 × 8 = 40 Marks)

Answer all Questions


Marks BL CO

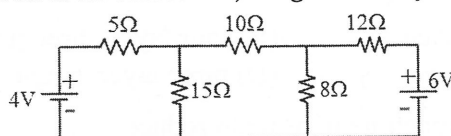- 21.a. Determine the value of current in the 8Ω resistor, using mesh analysis for the given circuit.



(OR)

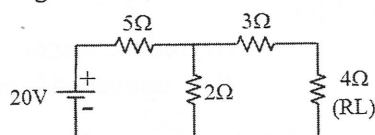- b. Define Thevenin's theorem. And find the current flow through the load resistance R_L using Thevenin's theorem in the circuit given below.




22. (a) With a neat diagram, explain in detail about the construction, working and characteristics of Bipolar Junction Transistor 8 5 2
(OR)
(b) Design a logic circuit that consists of 4 inputs (A, B, C, D) and two outputs. Output F1=1 if the input binary number is 9 or more than 9. Output F2=1 if the input binary number is 5 or less than 5.
23. (a) With neat sketch, explain the construction and working of servo motor. 8 3 3
(OR)
(b) Explain the principle, construction and working of induction motor with a neat diagram
24. (a) Illustrate the construction and working of LVDT and mention its advantages and disadvantages 8 3 4
(OR)
(b) Explain the construction and working of photo voltaic cell with a neat sketch
25. (a) Explain the need of Smart grid and its operation . 8 3 5
(OR)
(b) Explain the different Types of Earthing with a neat diagram

PART - C (1 × 15 = 15 Marks)

Answer any 1 Questions

Marks BL CO

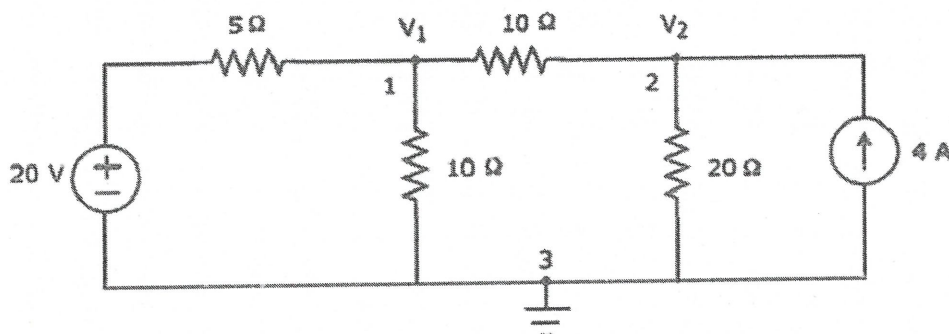26. Find the value of V1 and V2 using Nodal Analysis. 15 5 1



27. Using the K-map method obtain the minimal SOP & POS expressions for the function $F(x,y,z,w) = \sum(1,3,4,5,6,7,9,12,13)$ 15 5 2
